

## Sequential logic


Here the timing or sequencing of the input signals is important

e.g. Flip Flops, counters, latches, microprocessors.

---


Sequential logic responds to inputs only when a separate trigger signal transitions from one level to another  
this trigger is the CLOCK (ck) signal

Clock pulse edges

 

positive edge triggered

Negative edge triggered

 

Two types of edge triggered devices

1) Positive edge triggered  $CK = 1$


2) Negative edge triggered  $CK = 0$

↑ Input to  
Sequential  
logic gates


# Flip-Flops

Is a sequential logic device that can store data and switch between states (0/1).

## ① RS Flip-Flop

 

Positive edge-triggered

 

Negative edge-triggered.

Inputs

- S: set pin
- R: reset pin

Outputs

- Q,  $\bar{Q}$

▷ CK: Clock / positive edge-trigger

◁ CK: Clock / Negative edge-trigger

There are 2 aspects to Flip-Flop

① Truth Table


S	R	Q	$\bar{Q}$	Comments
→ 0	0	$Q_0$	$\bar{Q}_0$	Output Q is unchanged
→ 1	0	1	0	Set
0	1	0	1	Reset
x	x	Not available		$R = S = 1$ not allowed.

② The output  $Q, \bar{Q}$  will change when  $S, R$  are changed ONLY when CK or CLOCK has the correct trigger

# Illustration

Case 1 Positive edge triggered RS  
Flip-Flop. It is in the state


$$Q = 0 \quad / \quad \bar{Q} = 1$$

 

# Illustration

Case 1 Negative edge triggered RS Flip-Flop. It is in the state


$$Q = 0 / \bar{Q} = 1$$

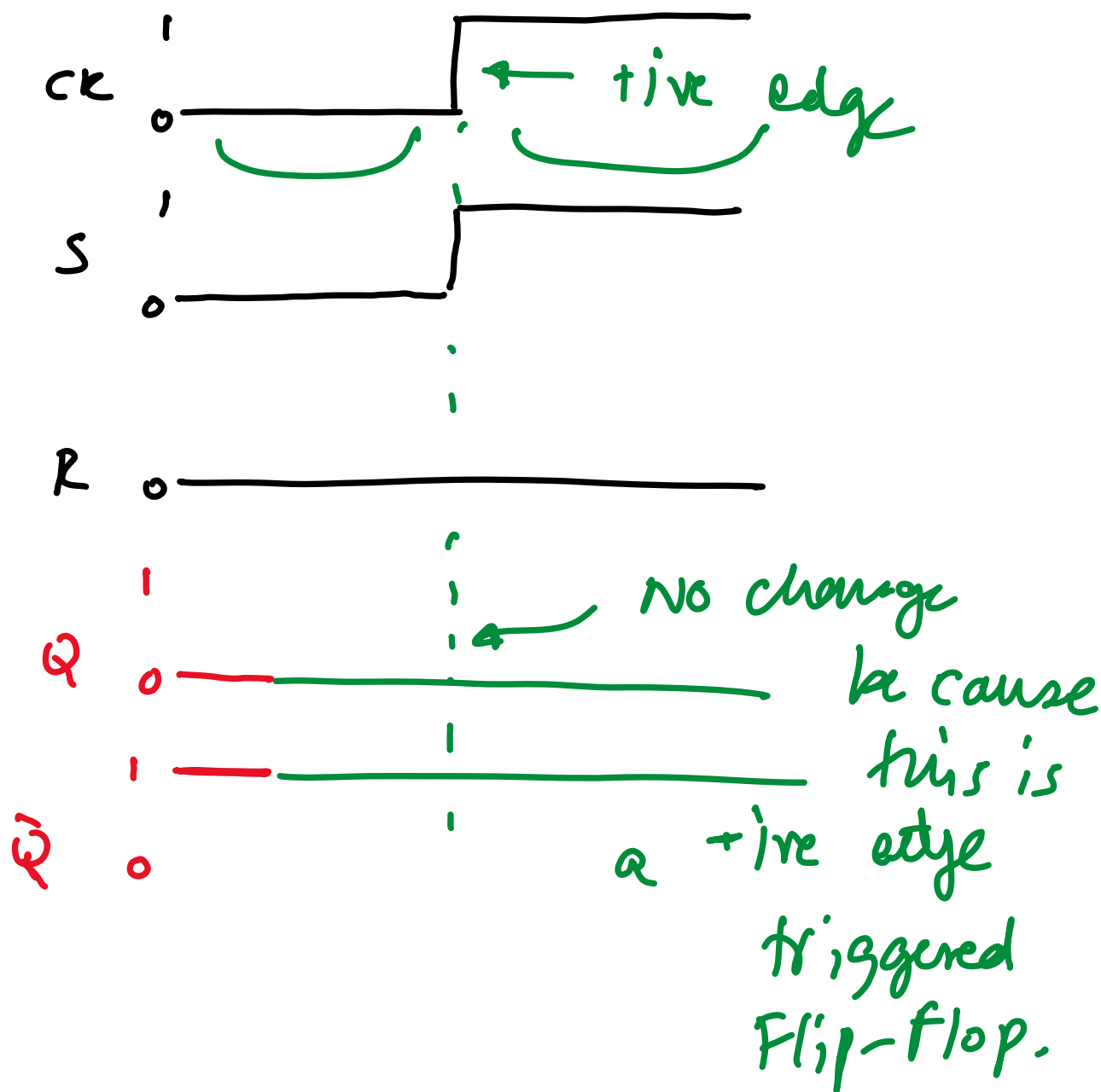


# Latch


Is a level triggered flip-flop.

↳ 0 or 1

 


Example: Positive level trigger

 

 



# D Flip-Flop

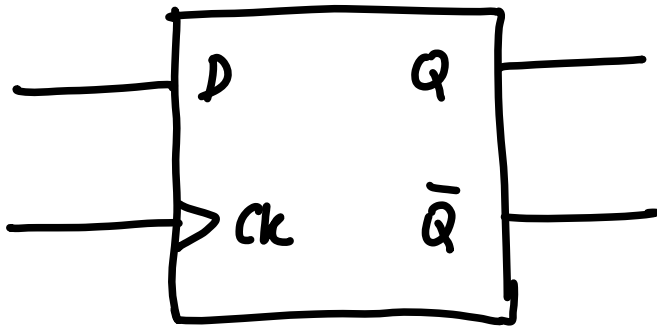

positive-edge  
trigger

D	ck	Q	$\bar{Q}$
0	↑	0	1
1	↑	1	0
X	0, 1, ↓	$Q_0$	$\bar{Q}_0$

X  
↓  
0 or 1

## ④ JK Flip-Flop


~ similar to RS Flip-Flop

JK in place of RS

~ R & S cannot be high simultaneously

J & K can be high "

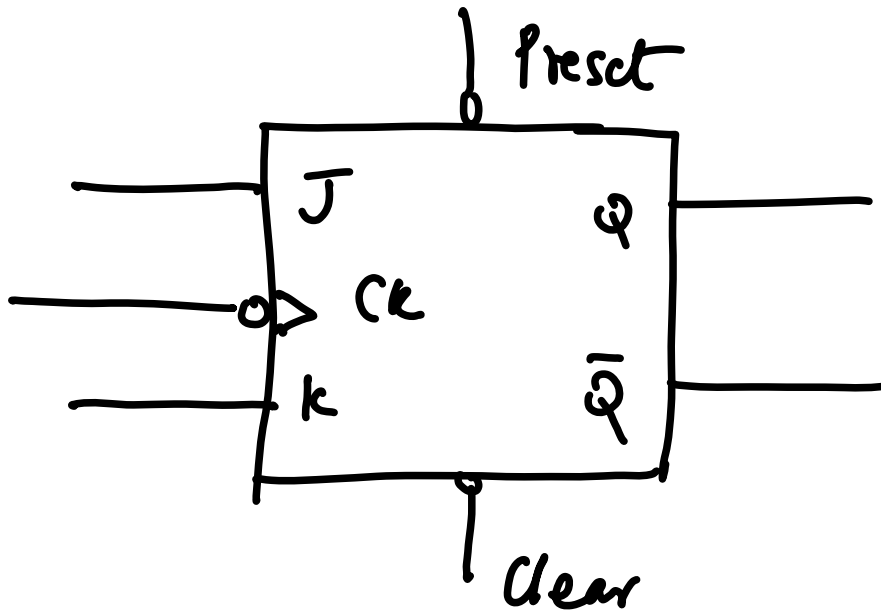~ Preset & Clear pin to initialize the state



5 inputs J, K, CK, Preset, Clear.


2 outputs Q,  $\bar{Q}$

$\overline{\text{Preset}}$	$\overline{\text{Clear}}$	CK	J	K	Q	$\overline{Q}$	
0	1	X	X	X	1	0	} Initialize
1	0	X	X	X	0	1	
0	0	—	Not available		—	—	} Not permitted
1	1	↓	0	0	$Q_0$	$\overline{Q_0}$	} Useful Inputs
1	1	↓	1	0	1	0	
1	1	↓	0	1	0	1	
1	1	↓	1	1	$\overline{Q_0}$	$Q_0$	
1	1	↑, 0, 1	X	X	$Q_0$	$\overline{Q_0}$	} Unchanged

Incorrect trigger  
↓ ↓ 0/1

All Flip-Flops can be constructed using JK Flip-Flops.

# T or Toggle Flip-Flop

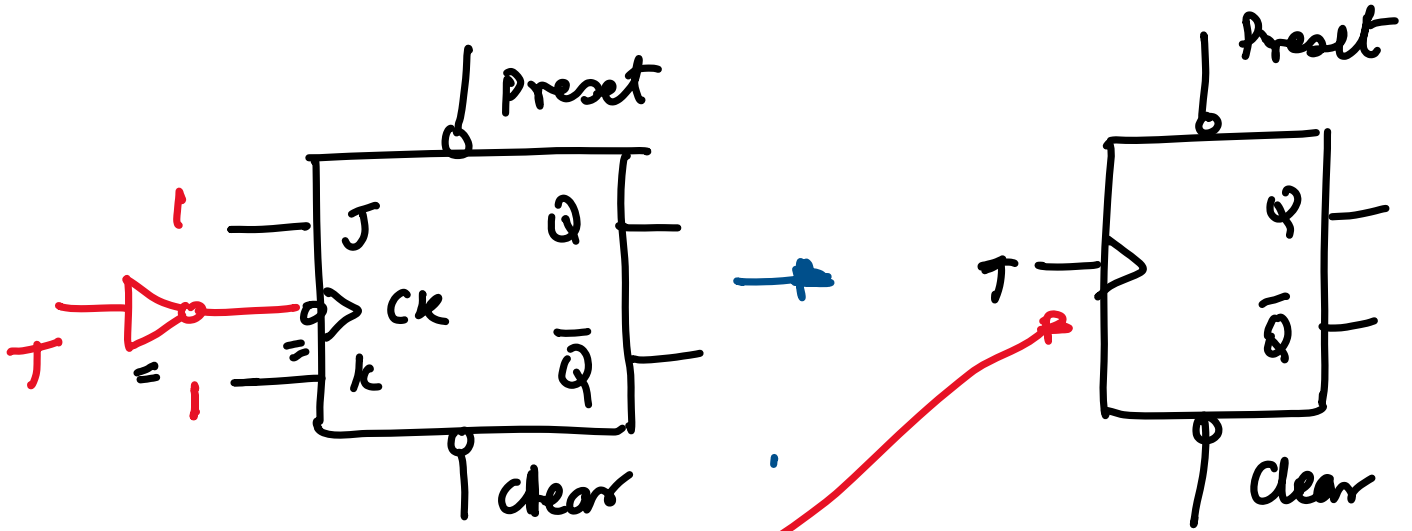

*True edge*

T	Preset	Clear	Q	$\bar{Q}$	
$\uparrow$	1	1	$\bar{Q}_0$	$Q_0$	<i>toggle</i>
0, 1, $\downarrow$	1	1	$Q_0$	$\bar{Q}_0$	<i>unchanged</i>
0, 1, $\downarrow, \uparrow$	0	1	1	0	} <i>Initialize</i>
0, 1, $\downarrow, \uparrow$	1	0	0	1	

*Does not depend on these inputs*